



SEMESTER END EXAMINATIONS - MARCH 2024


Program	: B.E. - Electronics and Communication Engineering	Semester	: III
Course Name	: Analog Electronics Circuits	Max. Marks	: 100
Course Code	: EC33	Duration	: 3 Hrs

Instructions to the Candidates:

- Answer one full question from each unit.

UNIT - I


- Derive the expressions for current gain (A_i), input impedance (Z_i), voltage gain (A_v), and output impedance (Z_o) of a transistor in Common Emitter (CE) configuration using the h-parameter model. CO1 (08)
 - With no feedback, a voltage amplifier exhibits the following parameters: Open circuit voltage gain (A) = -500; Input resistance (R_i) = 2 K Ω ; Output resistance (R_o) = 3 K Ω ; Bandwidth (BW) = 300 KHz. Upon applying a 10% negative voltage series feedback, calculate the feedback parameters: Feedback voltage gain (A_{vf}), Feedback input resistance (R_{if}), Feedback output resistance (R_{of}), and Feedback bandwidth (BW_f). CO1 (04)
 - Emphasize the significance of tank circuits and discuss the operational principles of a Transistorized Hartley oscillator with relevant illustrations. Subsequently, find the oscillation frequency in such an oscillator, if the inductor values are 5mH and 2mH and the capacitor value is 0.47 μ F. CO1 (08)
- Examine a single-stage Common Emitter (CE) amplifier depicted in the given figure shown below, with the following component values: $R_s = 1\text{K}\Omega$, $R_1 = 50\text{K}\Omega$, $R_2 = 2\text{K}\Omega$, $R_c = 1\text{K}\Omega$, $R_L = 1.2\text{K}\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1\text{K}\Omega$, $h_{oe} = 25 \mu\text{A/V}$, and $h_{re} = 2.5 \times 10^{-4}$. Calculate the amplifier parameters: Current gain (A_i), Input resistance (R_i), Voltage gain (A_v), and Output resistance (R_o and R_o'). CO1 (10)

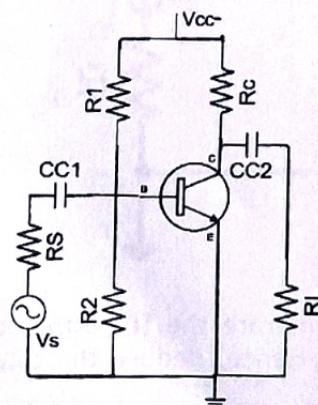

- Enumerate the effect of negative feedback on the input, and output impedance of a voltage series feedback amplifier with necessary expressions. CO1 (06)
- With a neat block diagram, explain the concept of oscillators and state the Barkhausen criterion for sustained oscillations. CO1 (04)

UNIT - II

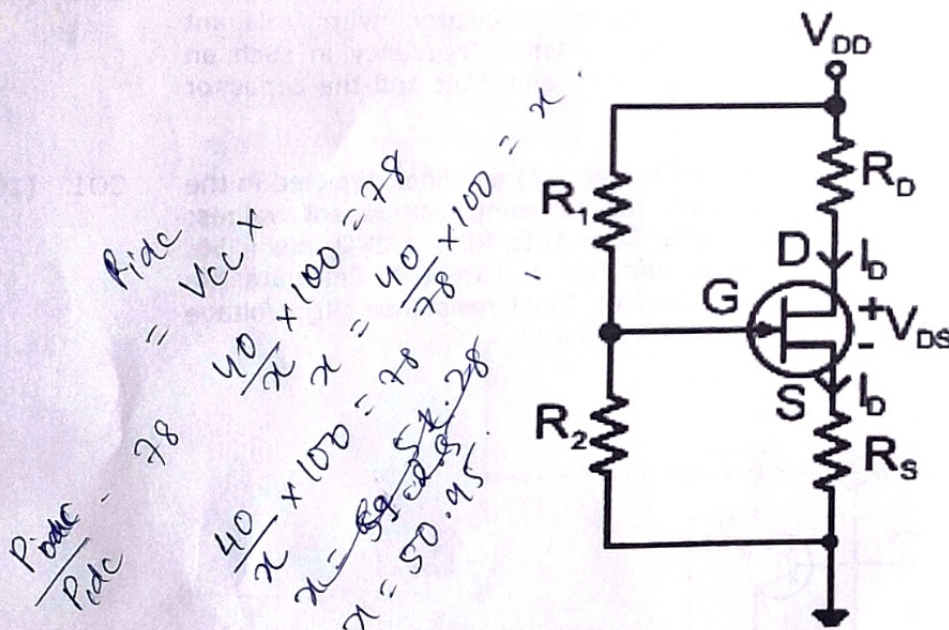3. a) Show that a transformer coupled Class A power amplifier has maximum conversion efficiency of 50%. CO2 (06)
- b) For a class B amplifier, providing a 20V peak signal to a 16Ω load and which has a power supply of 30V, determine (i) Input Power (ii) Output Power (iii) Circuit Efficiency (iv) maximum input power (v) Maximum Output Power (vi) Power dissipation across each transistor. CO2 (08)
- c) How does the JFET self-bias configuration work, and derive the expressions for the gate-to-source voltage, drain voltage, source voltage, and drain-source voltage in this configuration? CO2 (06)
4. a) Describe the functioning of a Class B push-pull amplifier, illustrating its operation through a circuit diagram and relevant waveform diagrams. CO2 (06)
- b) In an ideal class B push-pull power amplifier with input and output transformers (where $V_{cc} = 20V$, $N_2 = 2N_1$, $R_L = 20\Omega$, and transistors' $h_{fe} = 20$), and considering a sinusoidal input with the maximum output signal at $V_p = V_{cc}$, calculate the output signal power, power dissipation in each transistor, and the conversion efficiency. CO2 (04)
- c) Find the following parameters for the depicted figure shown below: CO2 (04)
 - (i) Drain current (I_D); (ii) Gate Voltage (V_G); (iii) Source voltage (V_s);
 - (iv) Gate source Voltage (V_{GS}), given: $V_{DD} = 12V$; $V_D = 7V$; $R_D = 3.3K\Omega$; $R_s = 1.8K\Omega$; $R_1 = 6.8K\Omega$; $R_2 = 1M\Omega$.



- d) Define harmonic distortion and enumerate the II harmonic distortion mathematically in Power amplifiers. Hence, deduce the total power in terms of total harmonic distortion. CO2 (06)

UNIT - III

5. a) Derive the expression for A_v , Z_i and Z_o of JFET common source amplifier with un bypassed R_S . CO3 (10)

- b) Determine Z_i , Z_o , and A_v for the network of Fig. 5(b) if $r_d = 60 \text{ k}\Omega$.

CO3 (10)

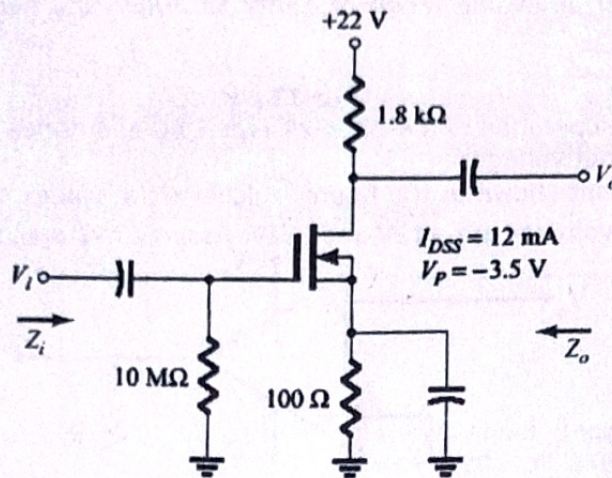


Fig. 5(b)

6. a) Derive the expression for A_v , Z_i and Z_o of JFET common drain amplifier.
b) Determine Z_i , Z_o , and V_o for the network of Fig. 6(b) if $V_i = 20 \text{ mV}$.

CO3 (10)

CO3 (10)

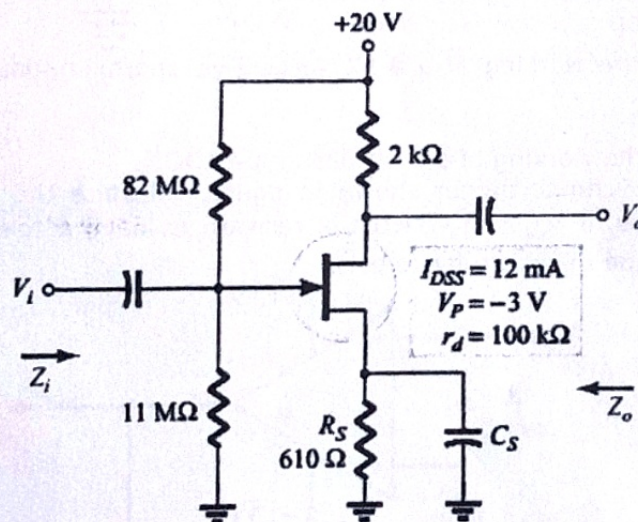


Fig. 6(b)

UNIT- IV

7. a) With a neat circuit diagram and expressions, explain the operation of a difference amplifier. Also discuss about its input resistances, common mode voltages and output level shifting. CO4 (06)
b) Define CMRR of an operational amplifier. An LM308 op-amp circuit with closed loop gain of 30 has a common mode input of 1 volt. Calculate the maximum output voltage this might produce. The minimum CMRR of LM308 is 80dB. CO4 (06)
c) Explain the working of a complete instrumentation amplifier with relevant circuits and expression. CO4 (08)
8. a) Draw the modified version of a sample and hold circuit with FET switch and Op-amps. Explain with waveforms. CO4 (08)
b) Design a first order low pass active filter with cut-off frequency of 2KHz. Use 741 op-amp. CO4 (06)